



Centurion
UNIVERSITY

Shaping Lives...
Empowering Communities...

Architecture Area, Speed & Power




Centurion
UNIVERSITY

Shaping Lives
Empowering Communities...

Two Always Block FSM Style (Good Style)

 One of the best Verilog coding styles is to code the FSM design using *two always blocks*, one for the *sequential state register* and one for the *combinational next-state and combinational output logic*.



Centurion
UNIVERSITY

*Shaping Lives...
Empowering Communities...*

Two Always Block FSM Style (Good Style)

```
module fsm_4states  
    (output reg gnt,  
     input dly, done, req, clk, rst_n);  
  
    parameter [1:0] IDLE = 2'b00,  
                  BBUSY = 2'b01,  
                  BWAIT = 2'b10,  
                  BFREE = 2'b11;  
    reg [1:0] state, next;  
  
    always @(posedge clk or negedge  
            rst_n)  
        if (!rst_n) state <= IDLE;  
        else state <= next;
```



Centurion
UNIVERSITY

*Shaping Lives...
Empowering Communities...*

Two Always Block FSM Style (Good Style)

```
always @(state or dly or done or req) begin
next = 2'bx;
gnt = 1'b0;
case (state)
    IDLE : if (req) next = BBUSY;
           else next = IDLE;
    BBUSY: begin
           gnt = 1'b1;
           if (!done) next = BBUSY;
           else if ( dly) next = BWAIT;
           else next = BFREE;
           end
    BWAIT: begin
           gnt = 1'b1;
           if (!dly) next = BFREE;
           else next = BWAIT;
           end
    BFREE: if (req) next = BBUSY;
           else next = IDLE;
endcase end endmodule
```



Centurion
UNIVERSITY
*Shaping Lives...
Empowering Communities*

Making default *next* equal all X's assignment

Placing a default next state assignment on the line immediately following the always block sensitivity list is a very efficient coding style. This default assignment is updated by next-state assignments inside the case statement.

There are three types of default next-state assignments that are commonly used: (1) next is set to all X's, (2) next is set to a predetermined recovery state such as IDLE, or (3) next is just set to the value of the state register.

By making a default next state assignment of X's, pre-synthesis simulation models will cause the state machine outputs to go unknown if not all state transitions have been explicitly assigned in the case statement.

This is a useful technique to debug state machine designs, plus the X's will be treated as "don't cares" by the synthesis tool.

Some designs require an assignment to a known state as opposed to assigning X's. Examples include: satellite applications, medical applications, designs that use the FSM flip-flops as part of a diagnostic scan



Centurion
UNIVERSITY

*Shaping Lives,
Empowering Communities...*

One Always Block FSM Style (Avoid This Style!)

One of the most common FSM coding styles in use today is the one sequential always block FSM coding style.

For most FSM designs, the one always block FSM coding style is more verbose, more confusing and more error prone than a comparable two always block coding style.



Centurion
UNIVERSITY

*Shaping Lives...
Empowering Communities...*

One Always Block FSM Style:

```
module fsm_4states  
    (output reg gnt,  
    input dly, done, req, clk, rst_n);
```

```
    parameter [1:0] IDLE = 2'd0,  
    BBUSY = 2'd1,  
    BWAIT = 2'd2,  
    BFREE = 2'd3;
```

```
    reg [1:0] state;
```



One Always Block FSM Style:

Centurion
UNIVERSITY

Shaping Lives...
Empowering Communities...

```
always @(posedge clk or negedge rst_n)
```

```
if (!rst_n) begin
```

```
state <= IDLE;
```

```
gnt <= 1'b0;
```

```
end
```

```
else begin
```

```
state <= 2'bx;
```

```
gnt <= 1'b0;
```

```
case (state)
```

```
  IDLE : if (req) begin
```

```
    state <= BBUSY;
```

```
    gnt <= 1'b1;
```

```
  end
```

```
  else
```




One Always Block FSM Style

Centurion

UNIVERSITY

Shaping Lives...
Empowering Communities...

```
BBUSY: if (!done) begin
    state <= BBUSY;
    gnt <= 1'b1;
end
else if ( dly) begin
    state <= BWAIT;
    gnt <= 1'b1;
end
else state <= BFREE;
BWAIT: if ( dly) begin
    state <= BWAIT;
    gnt <= 1'b1;
end
else state <= BFREE;
BFREE: if (req) begin
    state <= BBUSY;
    gnt <= 1'b1;
end
else state <= IDLE;
endcase
end
endmodule
```



Onehot FSM Coding Style (Good Style)

Centurion
UNIVERSITY
Simplifying Lives...
Empowering Communities...

Efficient (small and fast) onehot state machines can be coded using an inverse case statement; a case statement where each case item is an expression that evaluates to true or false.

Reconsider the fsm_4state design shown.

The key to understanding the changes is to realize that the parameters no longer represent **state** encodings, they now represent an *index* into the **state** vector, and comparisons and assignments are now being made to single bits in either the **state** or **next**-state vectors.

Notice how the case statement is now doing a 1-bit comparison against the onehot state bit.



Onehot FSM Coding Style

```
module fsm_cc4_fp
(output reg gnt,
input dly, done, req, clk, rst_n);
```

Index into the state register, not state encodings

```
parameter [3:0] IDLE = 0,
                BBUSY = 1,
                BWAIT = 2,
                BFREE = 3;
```

Onehot requires larger declarations

```
reg [3:0] state, next;
```

```
always @(posedge clk or negedge rst_n)
if (!rst_n) begin
state <= 4'b0;
state[IDLE] <= 1'b1;
end
else state <= next;
```

Reset modification

```
always @(state or dly or done or req) begin
next = 4'b0;
gnt = 1'b0;
```

Must make all-0's assignment


case (1'b1)

```
case (1'b1) // ambit synthesis case = full, parallel
state[IDLE] : if (req) next[BBUSY] = 1'b1;
               else next[IDLE] = 1'b1;
state[BBUSY] : begin
gnt = 1'b1;
if (!done) next[BBUSY] = 1'b1;
else if (dly) next[BWAIT] = 1'b1;
else next[BFREE] = 1'b1;
end
state[BWAIT] : begin
```

state[current_state] case items

Add "full" & "parallel" case

Only update the next[next_state] bit

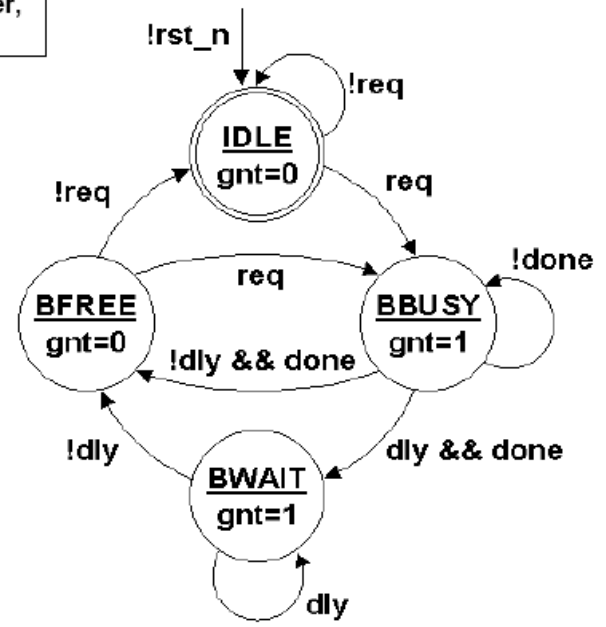



Centurion
UNIVERSITY

Shaping Lives...
Empowering Communities...

Onehot FSM Coding Style

```
state [BBUSY]: begin
    gnt = 1'b1;
    if (!done)
        next [BBUSY] = 1'b1;
    else if ( dly)
        next [BWAIT] = 1'b1;
    else
        next [BFREE] = 1'b1;
    end
state [BWAIT]: begin
    gnt = 1'b1;
    if (!dly)
        next [BFREE] = 1'b1;
    else
        next [BWAIT] = 1'b1;
    end
state [BFREE]: begin
    if (req)
        next [BBUSY] = 1'b1;
    else
        next [IDLE] = 1'b1;
    end
endcase
end
endmodule
```

state[current_state]
case items

Only update the
next[next state] bit



Centurion
UNIVERSITY

*She Dignifies Lives
Empowers the Commons...*

Onehot FSM Coding Style

This is the only coding style where one should use `full_case` and `parallel_case` statements.

The parallel case statement tells the synthesis tool to not build a priority encoder even though in theory, more than one of the state bits could be set

(as engineers, we should know that this is a onehot FSM and that only one bit can be set so no priority encoder is required).



Centurion
UNIVERSITY

*Shaping Lives...
Empowering Communities...*

Registered FSM Outputs (Good Style)

The Only Change one has to do is

always @(posedge clk or negedge rst_n)

if (!rst_n) gnt <= 1'b0;

else begin

gnt <= 1'b0;

case (next)

IDLE, BFREE: ; // default outputs

BBUSY, BWAIT: gnt <= 1'b1;

endcase

end

endmodule