

Power Dissipation

Where Does Power Go in CMOS?

- **Dynamic Power Consumption**

Charging and Discharging Capacitors


- **Short Circuit Currents**

Short Circuit Path between Supply Rails during Switching

- **Leakage**

Leaking diodes and transistors

Dynamic Power Dissipation

 


$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

- Not a function of transistor sizes!
- Need to reduce C_L , V_{dd} , and f to reduce power.

 Modification for Circuits with Reduced Swing




$$E_{0 \rightarrow 1} = C_L \cdot V_{dd} \cdot (V_{dd} - V_t)$$

- Can exploit reduced swing to lower power (e.g., reduced bit-line swing in memory)


Adiabatic Charging

Charging a capacitor

 


$$CV_{dd}^2/2$$

Consider

 

$$v_c = \frac{1}{C} \cdot \int_0^T i dt = \frac{1}{C} \cdot I_{av} \cdot T \quad I_{av} = \frac{C \cdot v_c}{T}$$


 
$$E_{dis} = R \cdot \int_0^T i^2 dt \geq R \cdot \int_0^T I_{av}^2 dt = R \cdot I_{av}^2 \cdot T = \frac{RC}{T} \cdot C \cdot V_c^2$$



Adiabatic Charging



$$V_I = RI + V_c = RC \frac{dv_c}{dt} + V_c$$

  $V_I = \text{cst} \rightarrow$ Exponential current



$$E_R = CV_c^2 / 2$$

  $I = I_{av} \rightarrow$ Linear ramp on V_I



wins if $T > 2RC$

minimal energy

$$E_R = RC/T CV_c^2$$

Node Transition Activity and Power

- Consider switching a CMOS gate for N clock cycles

$$E_N = C_L \cdot V_{dd}^2 \cdot n(N)$$

E_N : the energy consumed for N clock cycles


$n(N)$: the number of 0- \rightarrow 1 transition in N clock cycles

$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f_{clk} = \left(\lim_{N \rightarrow \infty} \frac{n(N)}{N} \right) \cdot C_L \cdot V_{dd}^2 \cdot f_{clk}$$

$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n(N)}{N}$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{dd}^2 \cdot f_{clk}$$

Transistor Sizing for Minimum Energy

 

- Goal: Minimize Energy of whole circuit
 - Design parameters: f and V_{DD}
 - $t_p \leq t_{pref}$ of circuit with $f=1$ and $V_{DD} = V_{ref}$

$$t_p = t_{p0} \left(\left(1 + \frac{f}{\gamma} \right) + \left(1 + \frac{F}{f\gamma} \right) \right)$$

$$t_{p0} \propto \frac{V_{DD}}{V_{DD} - V_{TE}}$$

Transistor Sizing (2)

□ Performance Constraint ($\gamma=1$)

$$\frac{t_p}{t_{pref}} = \frac{t_{p0}}{t_{p0ref}} \frac{\left(2 + f + \frac{F}{f}\right)}{(3 + F)} = \frac{V_{DD}}{V_{ref}} \frac{V_{ref} - V_{TE}}{V_{DD} - V_{TE}} \frac{\left(2 + f + \frac{F}{f}\right)}{(3 + F)} = 1$$


□ Energy for single Transition

$$E = V_{DD}^2 C_{g1} [(1 + \gamma)(1 + f) + F]$$


$$\frac{E}{E_{ref}} = \left(\frac{V_{DD}}{V_{ref}}\right)^2 \left(\frac{2 + 2f + F}{4 + F}\right)$$

Transistor Sizing (3)



$$V_{DD} = f(f)$$

 



$$E/E_{ref} = f(f)$$

 

Short Circuit Currents

  


How to keep Short-Circuit Currents Low?

  

Short circuit current goes to zero if $t_{\text{fall}} \gg t_{\text{rise}}$,
but can't do this for cascade logic, so ...

Minimizing Short-Circuit Power

 

- Keep the input and output rise/fall times the same (< 10% of Total Consumption)
from [Veendrick84]
(*IEEE Journal of Solid-State Circuits*, August 1984)
- If $V_{\text{dd}} < V_{\text{tn}} + |V_{\text{tp}}|$ then short-circuit power can be *eliminated!*