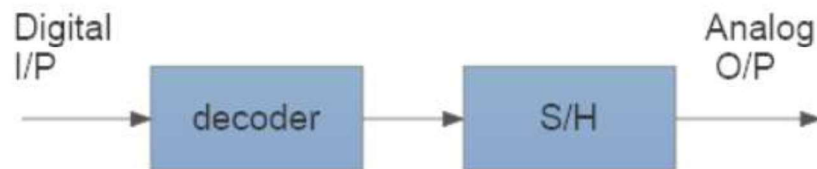



# Digital to Analog(D/A) conversion

- ▶ A digital to analog converter (DAC) converts a digital signal to an analog signal in form of voltage or current.
- ▶ Two methods:
  - Binary Weighted Resistor method and
  - R-2R Ladder


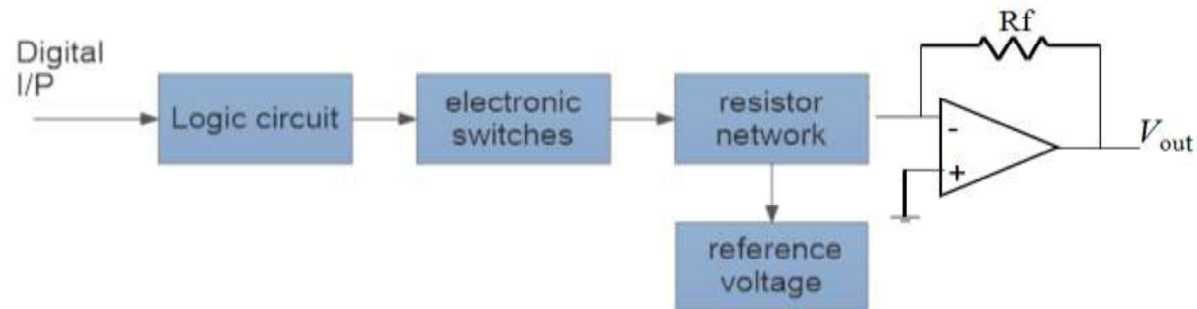
# Binary Weighted Resistor method

- ▶ Depending upon the digital input bit Logic circuit performs switching of resistor networks between  $V_{ref}$  and ground.
- ▶ Transistors are used to switch between  $V_{ref}$  and ground (bit high or low)
- ▶ weighted resistors are used to distinguish each bit from the MSB to LSB.



# Contd...

Resistors are connected to  $V_{ref}$  if corresponding bit is high or ground if corresponding bit is low

The output voltage is,


$$E_o = I_f R_f$$

If R is connected to  $E_r$ ,

$$E_o = \frac{E_r R_f}{R}$$

The general expression is,
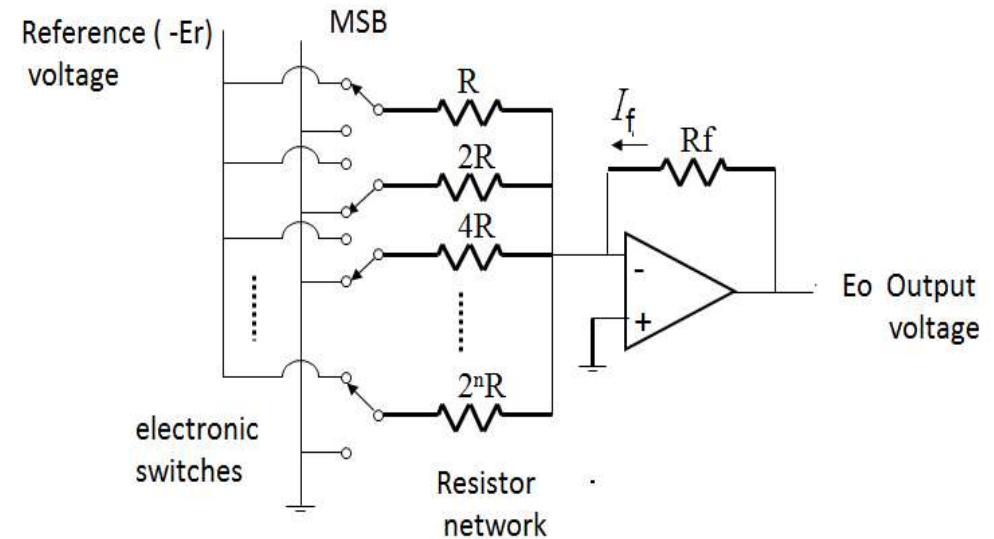
$$E_o = I_f R_f = \left( \frac{a_0}{R} + \frac{a_1}{2R} + \frac{a_2}{4R} + \Lambda + \frac{a_{n-1}}{2^{n-1} R} \right) R_f E_r$$



For a code of 1001

# Binary Weighted Resistor

- ▶ Advantages
  - Simple Construction/Analysis
  - Fast Conversion
- ▶ Disadvantages
  - A 10 bit DAC needs resistors ranging from  $R$  to  $R/1024$
  - Requires low switch resistances in transistors
  - Can be expensive. Therefore, usually limited to 8-bit resolution.

