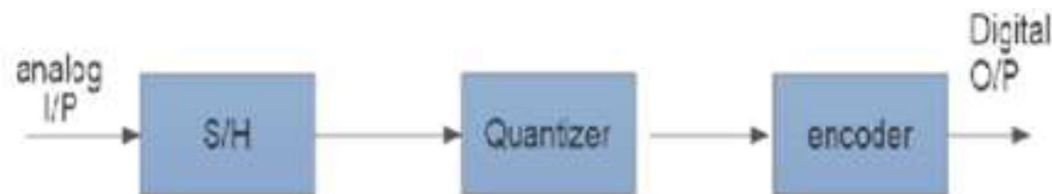


# Analog to Digital conversion

- ▶ An ADC converts analog signal to a digital coded signal.
- ▶ Types of Analog to Digital Converters
  - Successive Approximation
  - Counter Type
  - Integrating or Dual Slope
  - Parallel or Flash




# Analog → Digital Conversion

## Steps involved:

- ▶ Sampling – the analog signal is first sampled at periodic intervals.
- ▶ Quantizing – breaking down analog value into a set of finite states
- ▶ Encoding – assigning a digital word or number to each state and matching it to the input signal




# Successive Approximation method

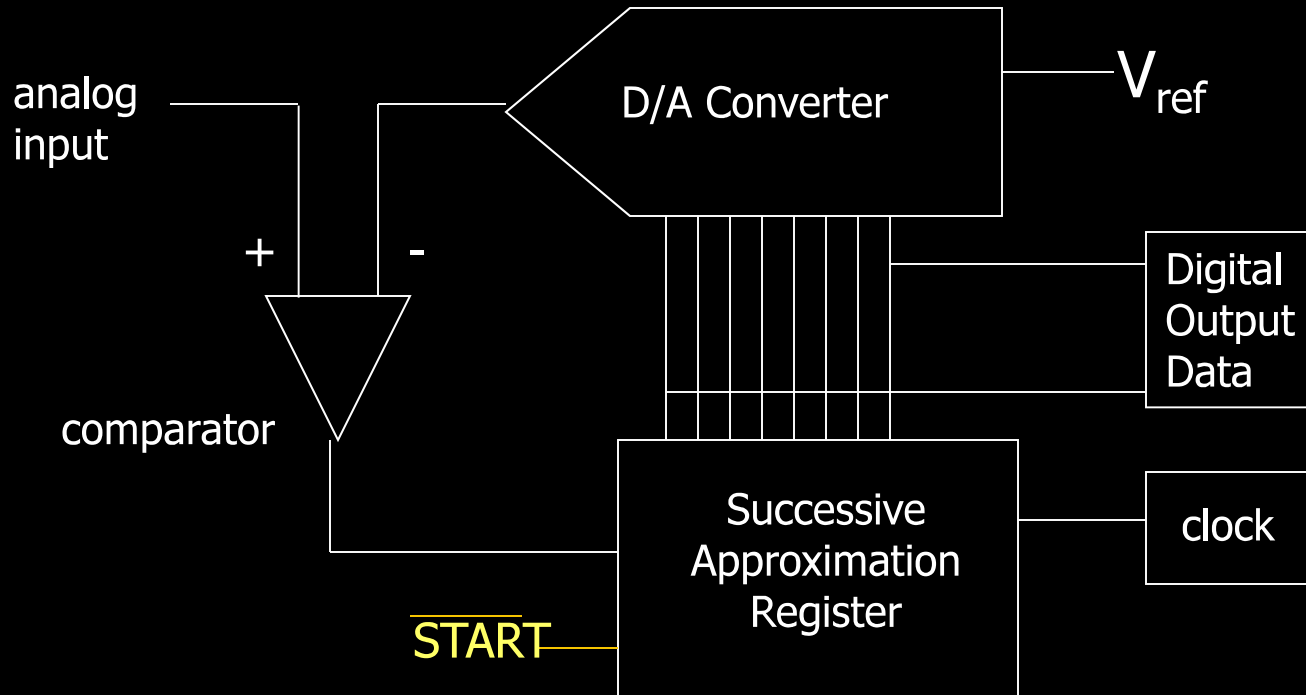


At initialization, all bits from the SAR are set to zero (clearing), and conversion begins by taking  $\overline{START}$  line low.

# Successive-Approximation A/D

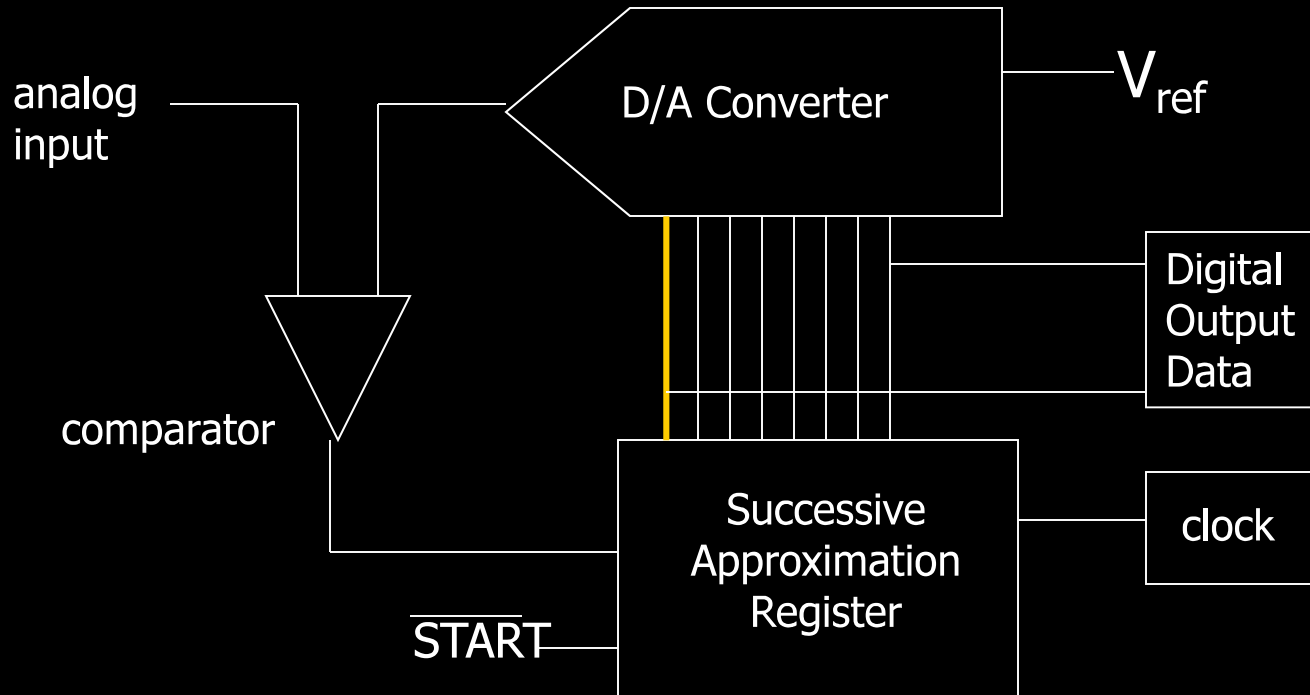


First the logic circuit in the SAR sets the MSB bit equal to 1 (+5 V). The MSB representing one half of full scale is converted by D/A converter.

# Successive-Approximation A/D

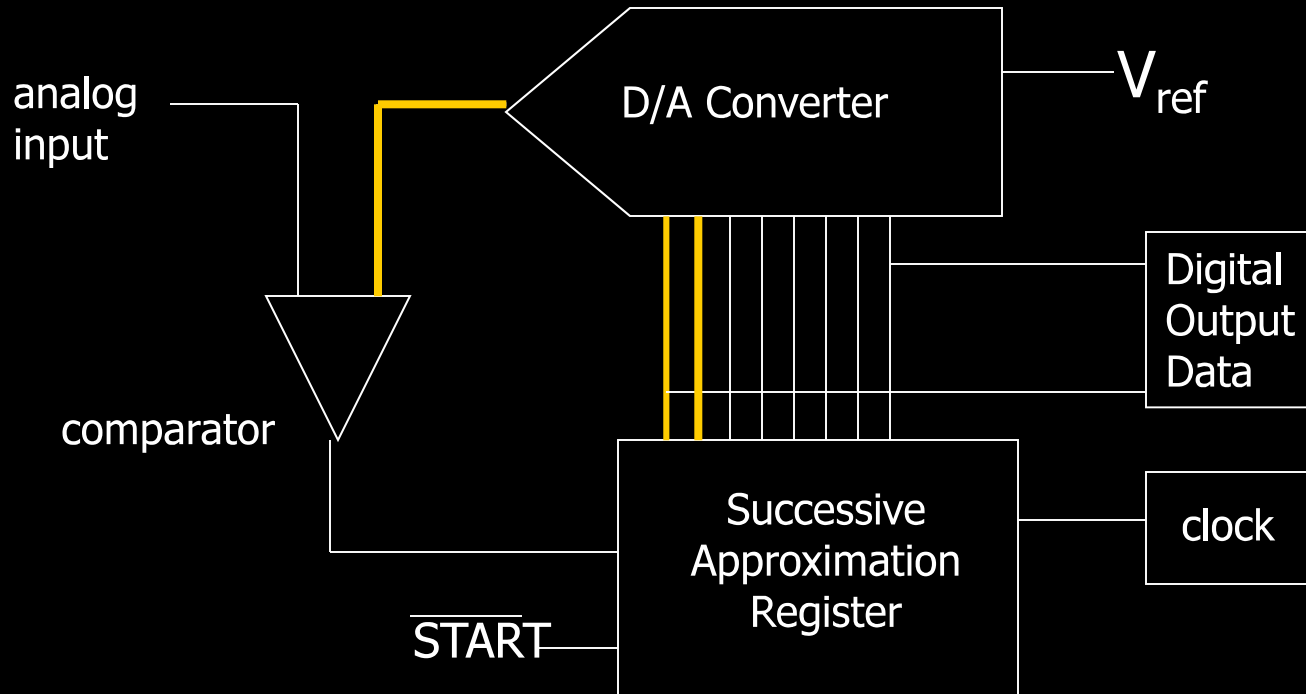


If the  $V_{in} >$  converted MSB then the MSB is left at 1 and the next bit is then tested.

# Successive-Approximation A/D

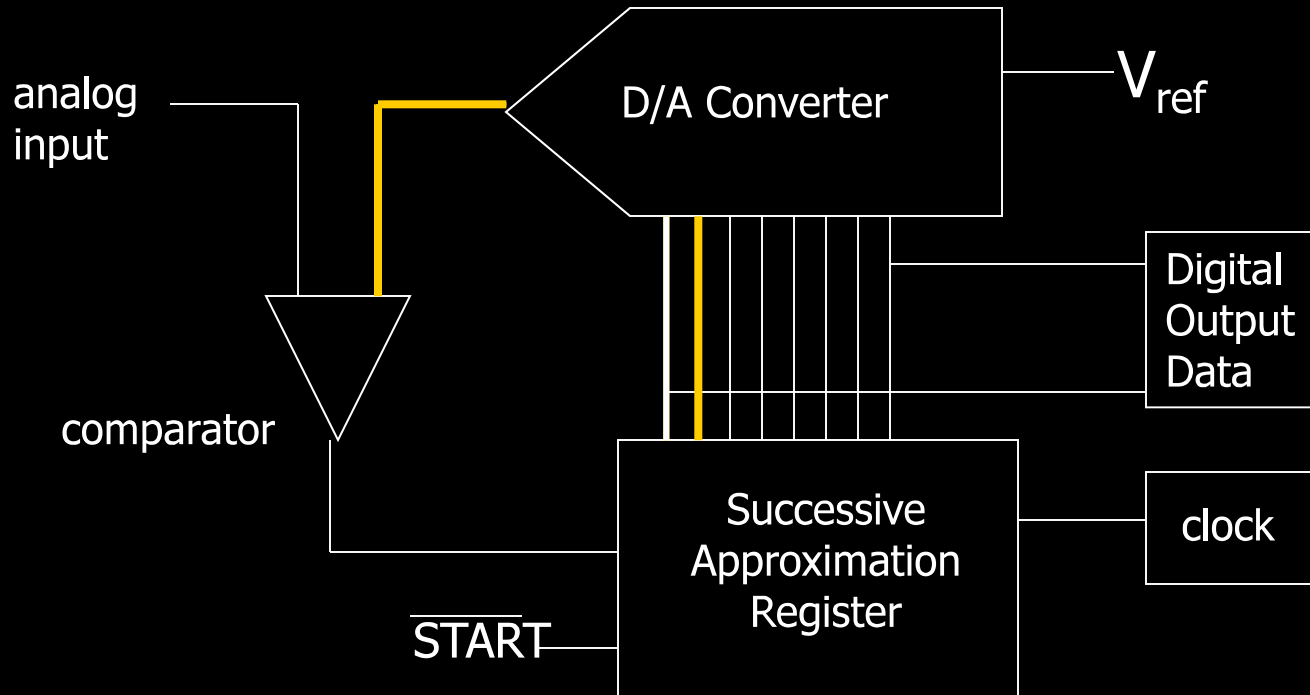

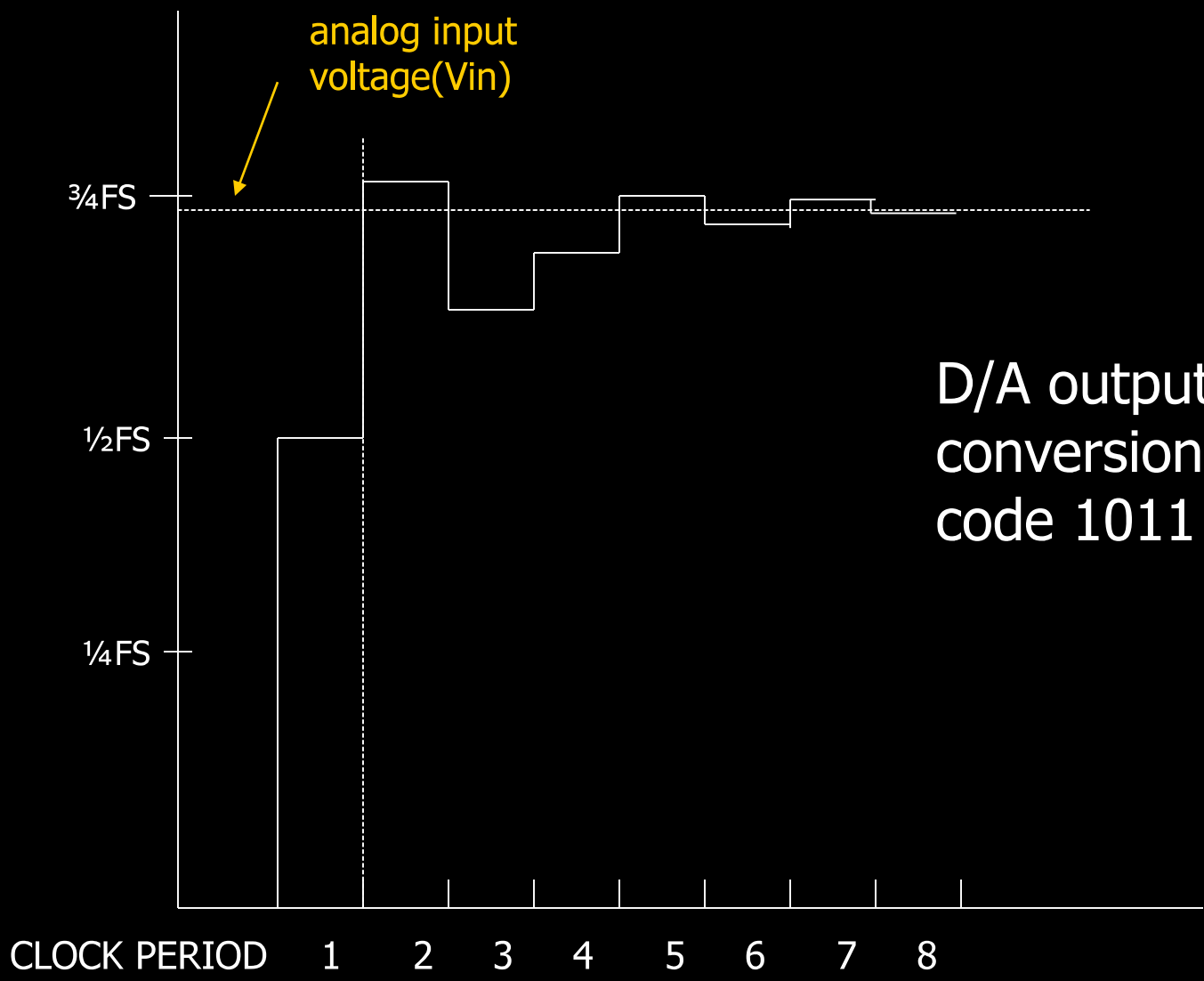If the  $V_{in} < \text{converted MSB}$  then the MSB is left at 1 and the next bit is then tested.



D/A output for 8-bit conversion with output code 1011 0101

# Successive Approximation

## Advantages

- ▶ Medium accuracy compared to other ADC types
- ▶ Capable of outputting the binary number in serial (one bit at a time) format.
- ▶ increasing the resolution which improves the accuracy
- ▶ increasing the sampling time which increases the maximum frequency that can be measured.

## Disadvantages

- ▶ Higher resolution successive approximation ADC's will be slower
- ▶ Speed limited to ~5Msps

