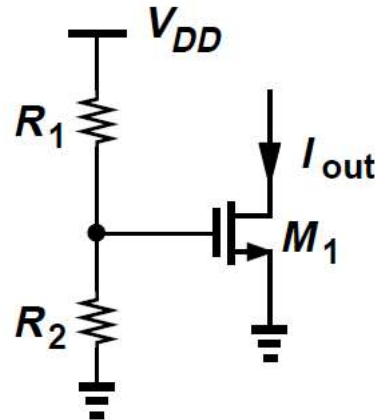


# Basic Current Mirrors

---





- Assuming  $M_1$  is in saturation, we can write

$$I_{out} \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2 .$$

- The threshold voltage may vary by 50 to 100 mV from wafer to wafer
- Both  $\mu_n$  and  $V_{TH}$  exhibit temperature dependence
- We must seek other methods of biasing MOS current sources.

# Conceptual means of copying currents

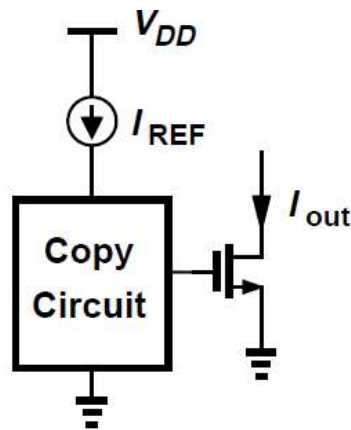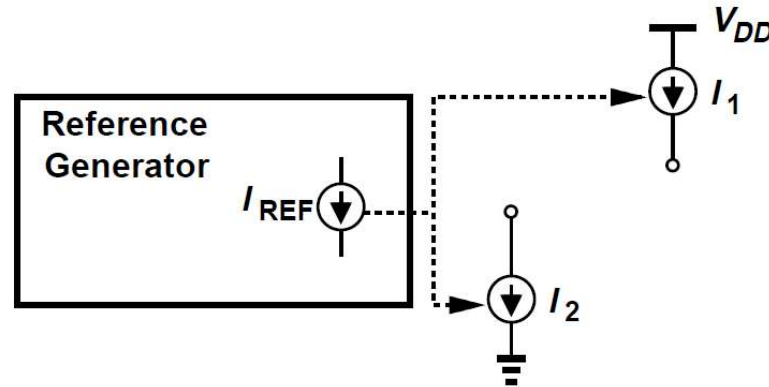


- Use of a reference to generate various currents.

$$I_{out} = f[f^{-1}(I_{REF})] = I_{REF}$$

- Two identical MOS devices that have equal gate-source voltages and operate in saturation carry equal currents

# Effect of Channel-Length Modulation

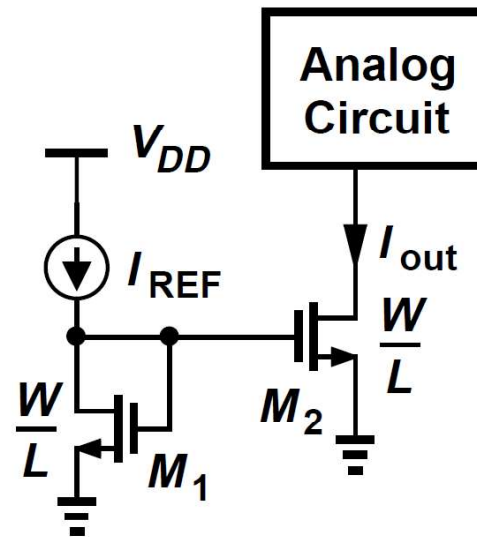

- Neglecting channel-length modulation, we can write


$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2$$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2,$$

$$I_{out} = \frac{(W/L)_2}{(W/L)_1} I_{REF}.$$

- Allows precise copying of the current with no dependence on process and temperature


# Sizing issues

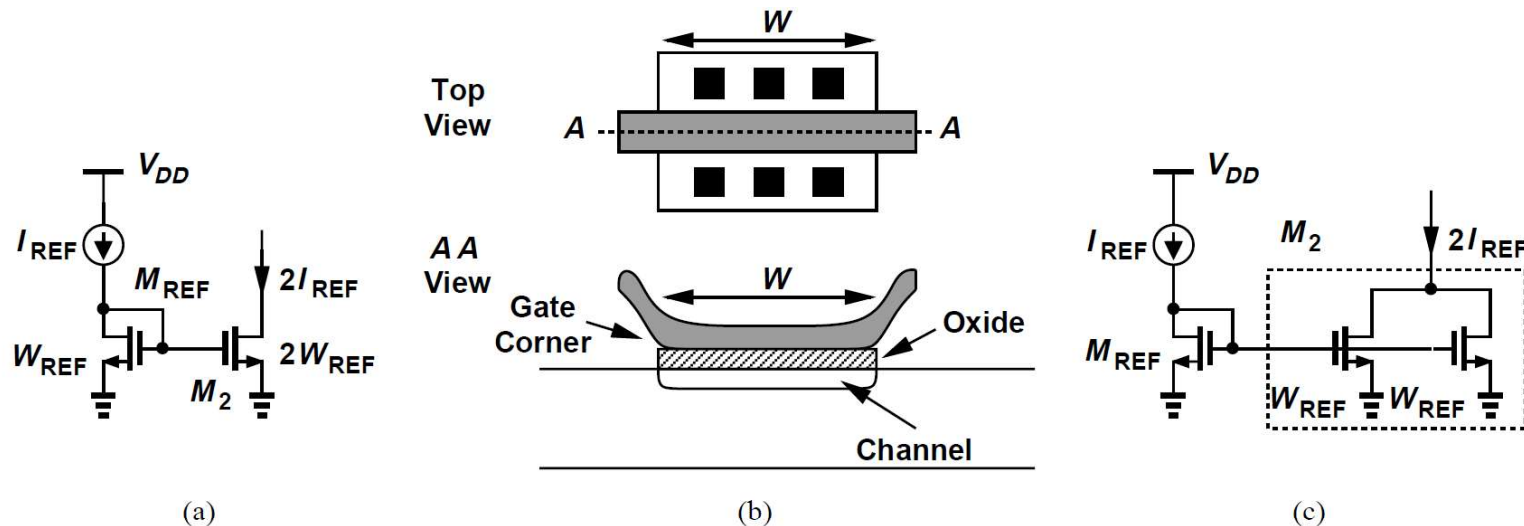

- Current mirrors usually employ the same length for all of the transistors.
- Current ratioing is achieved by only scaling the width of transistors.
- Direct scaling of the width also faces difficulties.
- We thus prefer to employ a “unit” transistor and create copies by repeating such a device.

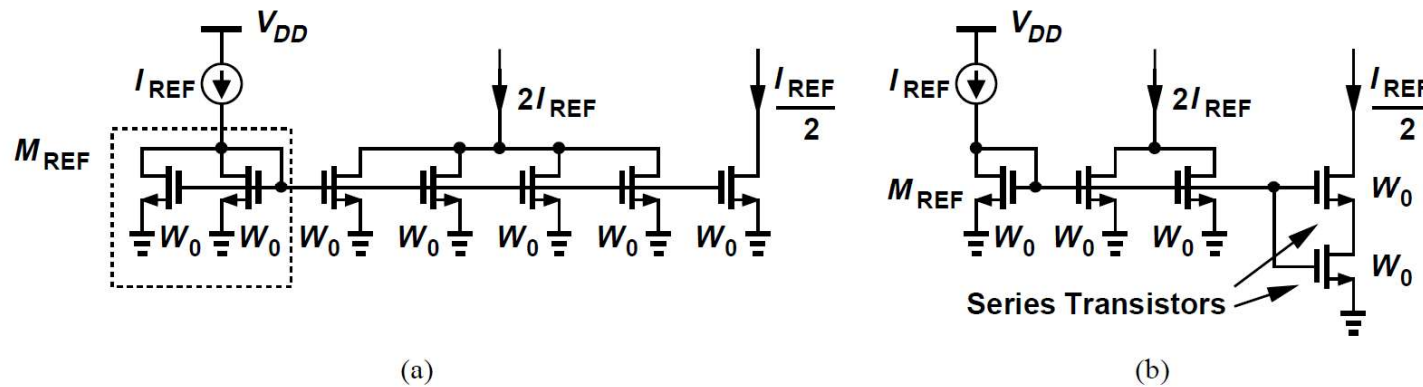
# Sizing Issues

- How do we generate a current equal to  $I_{REF} / 2 = 2$  from  $I_{REF}$  ?



- (a) half-width device, and (b) series transistors
- Approach (b) preserves an effective length of  $(L_{drawn} - 2L_D)$  for each unit, yielding an equivalent length of  $2(L_{drawn} - 2L_D)$
- Current mirrors can process signals as well, example next slide.

# Example

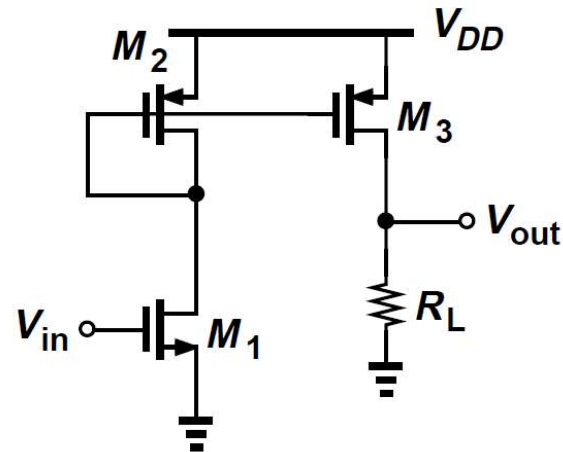


- Calculate the small-signal voltage gain of the circuit shown in Figure.

$$I_{D2} = I_{D1}$$

$$I_{D3} = I_{D2}(W/L)_3/(W/L)_2$$

- Gain=  $g_{m1}R_L(W/L)_3/(W/L)_2$

# Cascode Current Mirrors

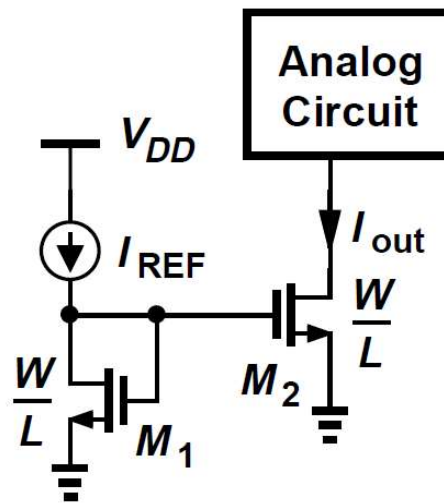


$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS1})$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS2})$$

$$\frac{I_{D2}}{I_{D1}} = \frac{(W/L)_2}{(W/L)_1} \cdot \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

- While  $V_{DS1} = V_{GS1} = V_{GS2}$ ,  $V_{DS2}$  may not equal  $V_{GS2}$
- We can (a) force  $V_{DS2}$  to be equal to  $V_{DS1}$ , or (b) force  $V_{DS1}$  to be equal to  $V_{DS2}$ .



# First Approach

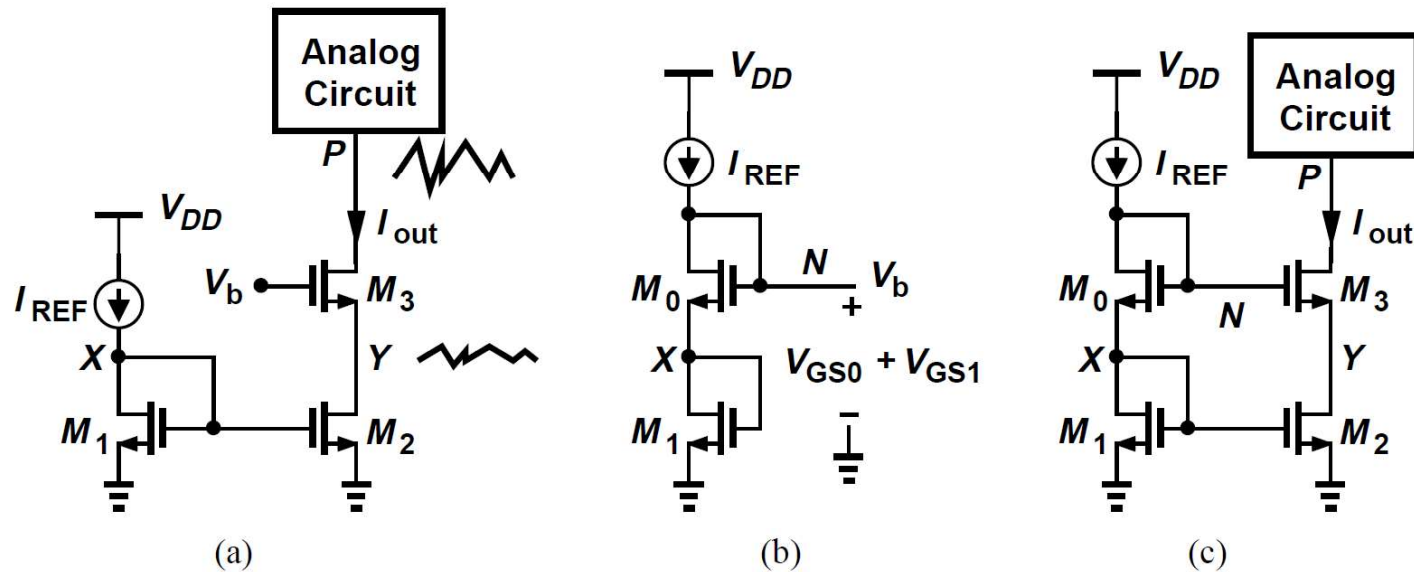

- A cascode device can shield a current source, thereby reducing the voltage variations across it.
- But, how do we ensure that  $V_{DS2} = V_{DS1}$ ?
- We must generate  $V_b$  such that  $V_b - V_{GS3} = V_{DS1}(= V_{GS1})$



# Example

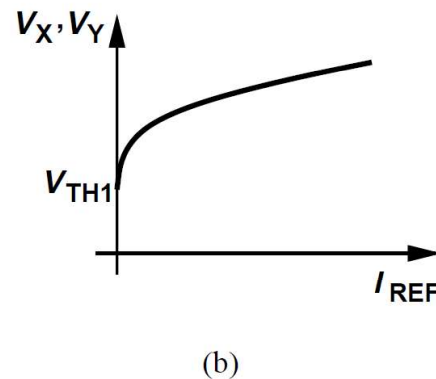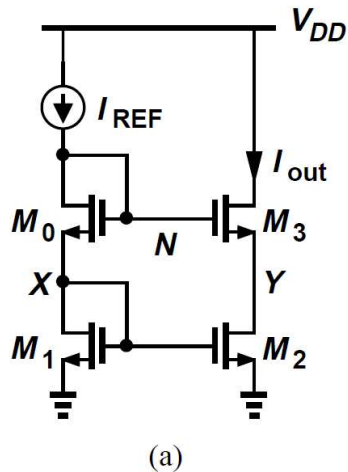

- sketch  $V_X$  and  $V_Y$  as a function of  $I_{REF}$ . If  $I_{REF}$  requires 0.5 V to operate as a current source, what is its maximum value?


$$V_Y = V_X \approx \sqrt{2I_{REF} / [\mu_n C_{ox} (W/L)_1]} + V_{TH1}$$

$$\begin{aligned} V_N &= V_{GS0} + V_{GS1} \\ &= \sqrt{\frac{2I_{REF}}{\mu_n C_{ox}}} \left[ \sqrt{\left(\frac{L}{W}\right)_0} + \sqrt{\left(\frac{L}{W}\right)_1} \right] + V_{TH0} + V_{TH1} \end{aligned}$$

$$V_{DD} - \sqrt{\frac{2I_{REF}}{\mu_n C_{ox}}} \left[ \sqrt{\left(\frac{L}{W}\right)_0} + \sqrt{\left(\frac{L}{W}\right)_1} \right] - V_{TH0} - V_{TH1} = 0.5 \text{ V}$$

$$I_{REF,max} = \frac{\mu_n C_{ox} (V_{DD} - 0.5 \text{ V} - V_{TH0} - V_{TH1})^2}{2 (\sqrt{(L/W)_0} + \sqrt{(L/W)_1})^2}$$


# Example

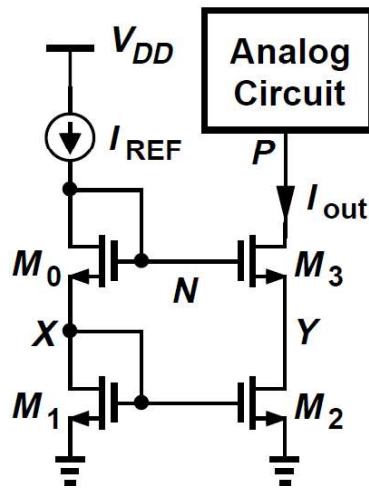


- the minimum allowable voltage at node P is equal to

$$\begin{aligned}V_N - V_{TH} &= V_{GS0} + V_{GS1} - V_{TH} \\ &= (V_{GS0} - V_{TH}) + (V_{GS1} - V_{TH}) + V_{TH}\end{aligned}$$

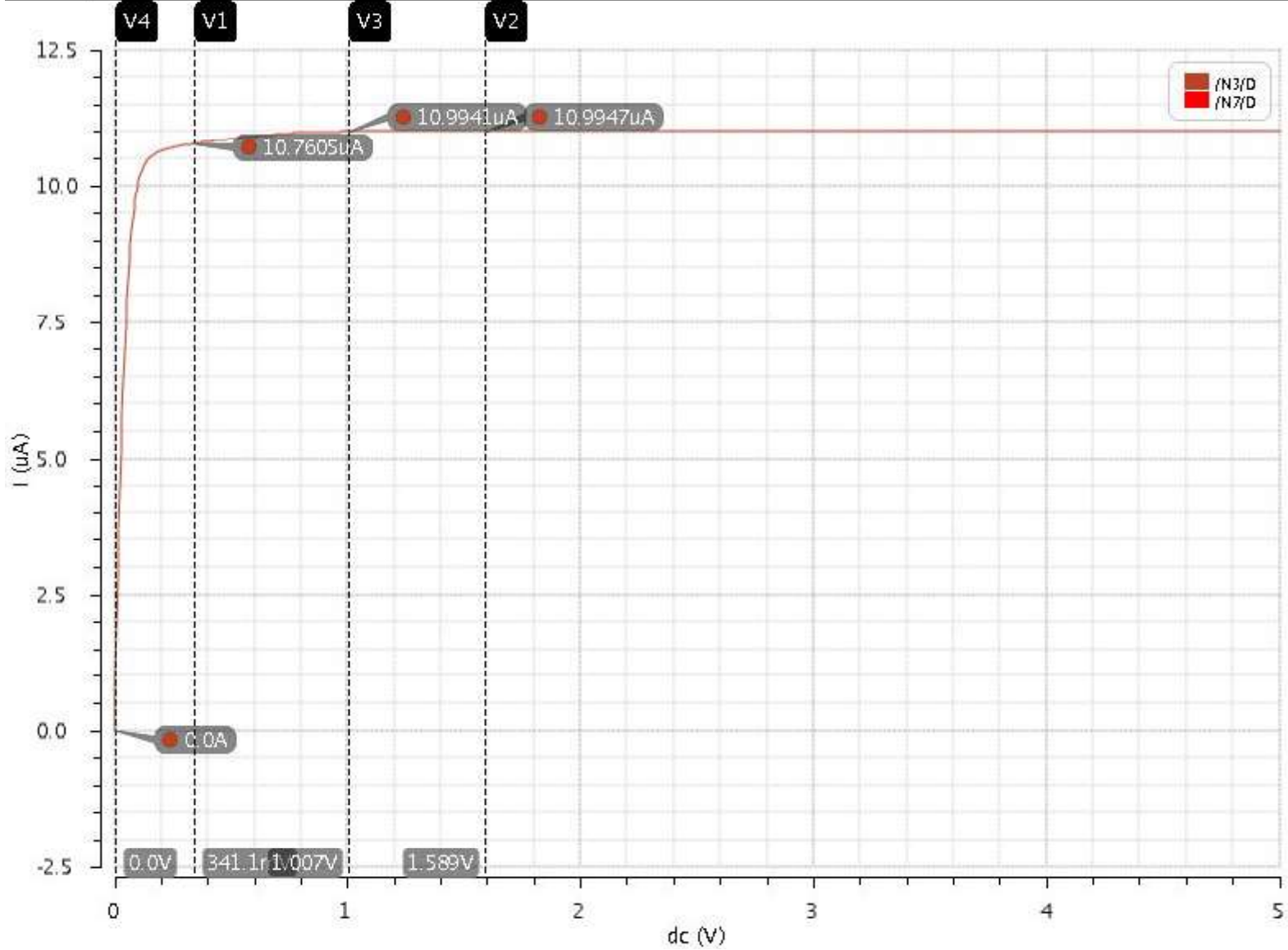- The cascode mirror “wastes” one threshold voltage in the headroom.
- Because  $V_{DS2} = V_{GS2}$ , whereas  $V_{DS2}$  could be as low as  $V_{GS2} - V_{TH}$  while maintaining M2 in saturation.




# Approach summary

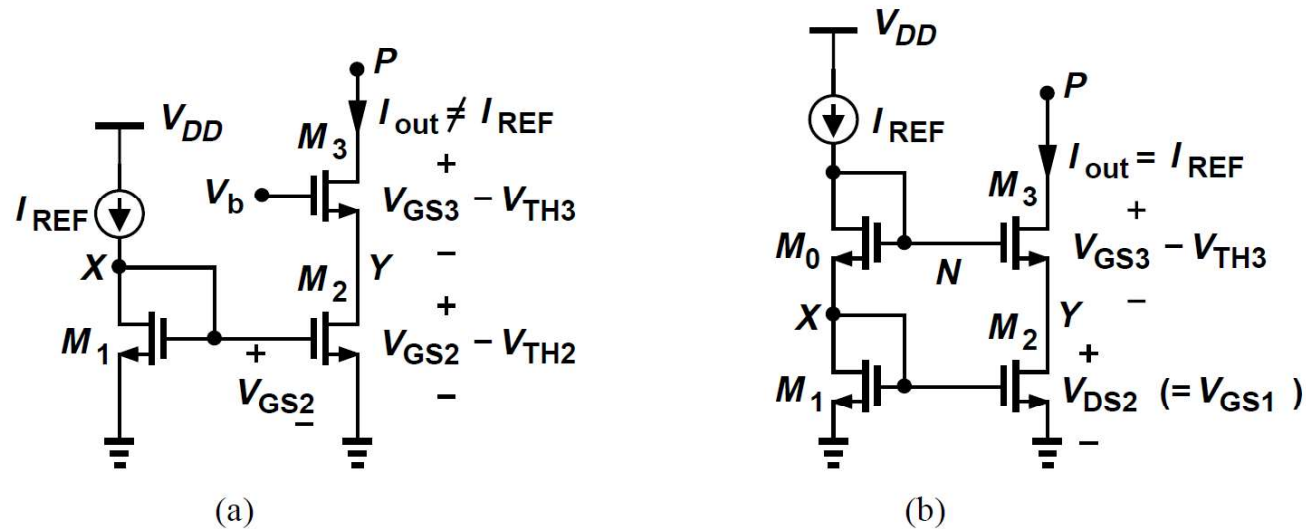

- In Fig(a),  $V_b$  is chosen to allow the lowest possible value of  $V_P$  but the output current does not accurately track  $I_{REF}$ .
- In Fig(b), a higher accuracy is achieved, but the minimum level at  $P$  is higher by one threshold voltage.

# Second Approach

---

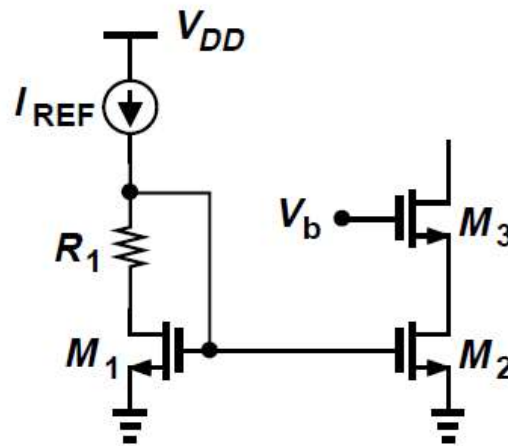


- Consider the branch shown in Fig. 5.16(b)
- As a candidate and write  $V_b = V_{GS5} + R_6 I_6$ .

$$R_1 I_{REF} \approx V_{TH1}$$

$$V_b = V_{GS3} + (V_{GS1} - V_{TH1})$$

# Small signal Model

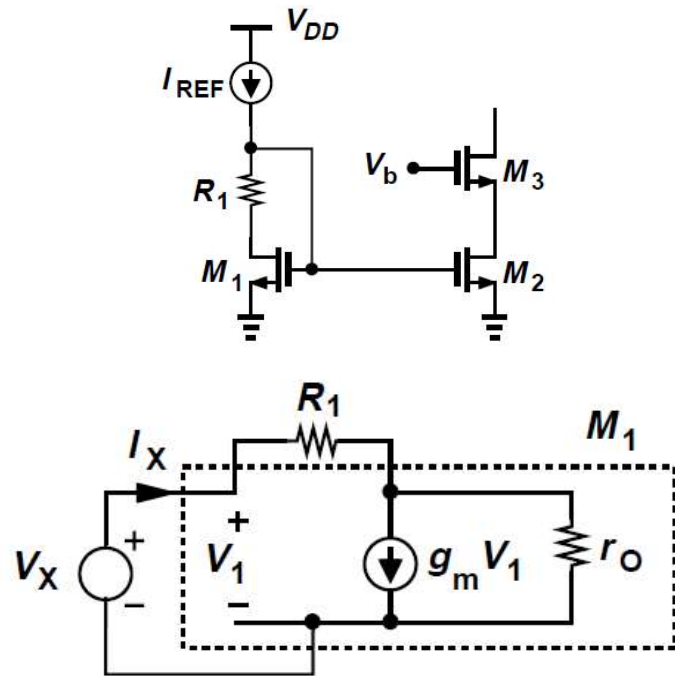


$$\frac{V_X - I_X R_1}{r_O} + g_m V_X = I_X.$$

$$\frac{V_X}{I_X} = \frac{R_1 + r_O}{1 + g_m r_O},$$


- Reduces to  $1/g_m$  in the absence of channel-length modulation.
- Thus, from a small-signal point of view, the combination is close to a diode-connected device.
- But
  - (1) It may be difficult to guarantee that  $R_1 I_{REF} \approx V_{TH1}$
  - (2) The generation of  $V_b = V_{GS3} + (V_{GS1} - V_{TH1})$  is not straightforward.

# Generate $V_b$

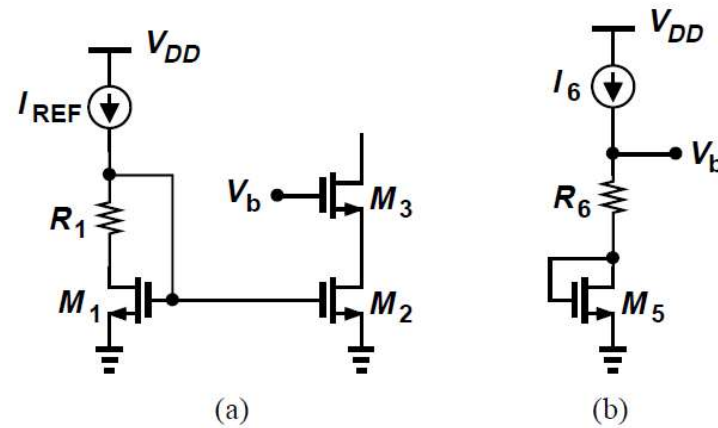

- Consider the branch shown in Fig(b) as a candidate and write  $V_b = V_{GS5} + R_6 I_6$ .
- $V_{GS5} = V_{GS3}$
- However, the condition  $R_6 I_6 = V_{GS1} - V_{TH1} = V_{GS1} - R_1 I_{REF}$  is hard to meet.

# Generate $V_b$

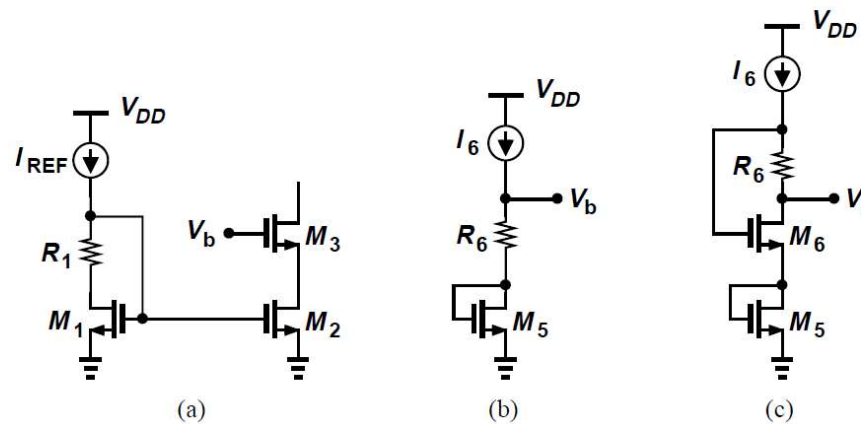


$$V_{GS5} = V_{GS3}$$

$$\begin{aligned} V_{GS6} - R_6 I_6 &= V_{GS1} - V_{TH1} \\ &= V_{GS1} - R_1 I_{REF} \end{aligned}$$

- It is now possible to ensure that  $V_{GS6}$  and  $V_{GS1}$  track each other.
- For example, we may simply choose  $I_6 = I_{REF}$ ,  $R_6 = R_1$ , and  $(W/L)_6 = (W/L)_1$



# Another circuit topology

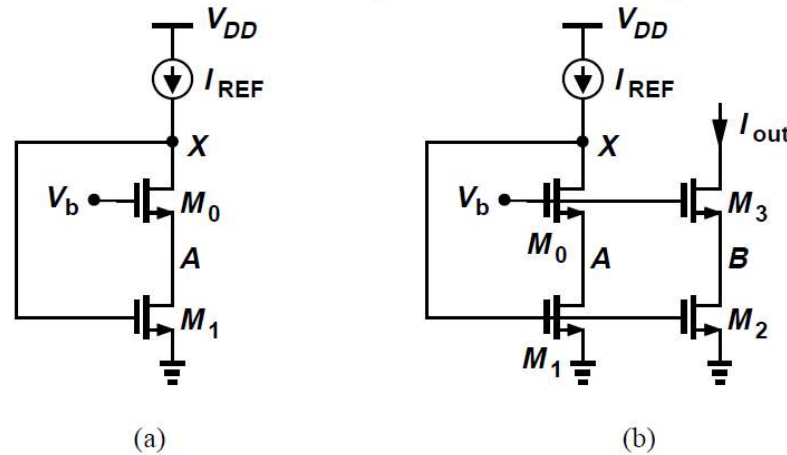

- In this case

$$V_{DS1} = V_b - V_{GS0}$$

- **Must have**  $V_b - V_{TH0} \leq V_X (= V_{GS1})$  **for M0 to be saturated** and  $V_{GS1} - V_{TH1} \leq V_A (= V_b - V_{GS0})$  **for M1 to be saturated.**
- **A solution exists if**  $V_{GS0} + (V_{GS1} - V_{TH1}) < V_{GS1} + V_{TH0}$
- **We must therefore size M0 to ensure its overdrive is well below  $V_{TH1}$ .**